Sea	ıt No.:	Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY M.E. SEMESTER III-EXAMINATION – WINTER 2015	_
Subject code: 2734501  Subject Name: Application of Power Electronics to Power System Time: 2:30 PM to 5:00 PM  Instructions:  1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.			15
Q.1	(a)	Explain basic construction, working and operating characteristic of Thyristor	07
	<b>(b)</b>	Control Reactor (TCR).  Draw the dynamic V-I characteristics for reduction in the SVC reactive-power rating by the current slope and explain it.	07
Q.2	(a)	Explain the principle of operation of basic Thyristor-Controlled Series Capacitor	07
	(b)	(TCSC) scheme.  Derive the ratio of reactive power compensation to be provided by a series compensator and a midpoint shunt compensator, to achieve the same change in active power transfer through a given transmission line. Assume identical voltages at respective ends of the line in both the cases. Calculate this ratio for a line operating with a 15° phase angle difference between the two ends.  OR	07
	<b>(b)</b>	Explain operating characteristics of FC-TCR without step-down transformer.	07
Q.3	(a) (b)	Discuss the role of SVC as a voltage controller.  Explain the principle of operation of Static Synchronous Series Capacitor (SSSC) scheme.	07 07
Q.3	(a) (b)	OR Explain load sharing between parallel connected SVCs with diagram Show that a TCSC compensated line could not cause or participate in a subsynchronous resonance. State the condition assumed for such property of TCSC based circuit.	07 07
Q.4	(a)	Using relevant phasor diagram and equations, explain how a shunt connected switching converter type var generator can be used as a bidirectional active-reactive power compensator based on the principle of operation of STATCOM.	07
	<b>(b)</b>	Explain principle of operation of UPFC with relevant phasor diagram and describe its implementation using back to back VSCs with schematic diagram OR	07
Q.4	(a)	Draw and explain the V-I characteristics of STATCOM and give a brief comparison with the V-I characteristics of TSC-TCR.	07
0.5	<b>(b)</b>	Explain the construction and working of a IPFC.	07
Q.5	(a) (b)	Explain the basic working principle of Thyristor Controlled Transformer. Explain synchronous reference frame theory.	07 07

\*\*\*\*\*

(a) Explain significance of reactive power control. Also Compare Series and Shunt Capacitor compensators.(b) Explain Instantaneous reactive power theory.

Q.5

OR

**07** 

**07**