Seat No.: ____

Enrolment No.___

GUJARAT TECHNOLOGICAL UNIVERSITY

M.E. SEMESTER I (old course)-EXAMINATION (Remedial) - WINTER 2015 Date: 14/12/2015

Subject code: 710305

Subject Name: Programmable Logic Controller

Time: 10:30 AM to 1:00 PM **Instructions:**

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a) (b)	Draw and explain block diagram of PLC. Discuss advantages and disadvantages of PLC.	07 07	
Q.2	(a) (b)	Develop the ladder diagram for 4 to 1 Multiplexer. Draw the ladder diagram for $F(a,b,c) = \Sigma(0,1,3,5,6,7)$ OR	07 07	
Q.3	(b)	Develop the ladder diagram for AND, OR, EX-OR Gate. Explain TON, TOF, RTO instruction of PLC with timing diagram. OR	07 14	
Q.3 Q.4	(a)	Explain PLC counter related instructions with suitable example. Develop a PLC program with start and stop button. Pressing a <i>START</i> will start the motor and <i>STOP</i> will stop the motor. Motor shall remain ON even if <i>START</i> button is depressed.	14 07	
	(b)	Explain various types of registers used in PLC.	07	
Q.4	(a) (b)	Explain PLC data comparison instructions. Explain PLC <i>arithmatic</i> function with suitable example.	07 07	
Q.5	(a) (b)	Explain PLC <i>skip</i> and <i>jump</i> functions. Prepare the ladder diagram to generate square wave pulse. OR	07 07	
Q.5	(a) (b)	Explain PLC Sequencer Functions with example, Write short note on types of networking.	07 07	
