

GUJARAT TECHNOLOGICAL UNIVERSITY**M.E. SEMESTER III–EXAMINATION (Remedial)– WINTER 2015****Subject code: 734501****Date: 04/12/2015****Subject Name: Application of Power Electronics to Power System****Time: 2:30 PM to 5:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Justify: Voltage Source Converter is building block of Flexible AC Transmission System. Draw necessary diagram in support. **07**
- (b) With the help of Phasor diagrams and mathematical equations explain conventional transmission capabilities of the Unified Power Flow Controller. **07**
- Q.2** (a) For a 400 kV, 50 Hz, 600 km long symmetrical line is operated at the rated voltage, determine: **07**
- (i) Theoretical maximum Power carried by the line. Also midpoint voltage corresponding to this condition.
- (ii) The reactance of a series capacitor, connected at the midpoint of the line double the power transmitted.
- Consider, $l = 1 \text{ mH/km}$ and $c = 11.1 \times 10^{-9} \text{ F/km}$
- (b) List various operating modes of Thyristor Controlled Series Capacitor for controlled series compensation. Also analyze the same for Vernier control operation. **07**
- OR**
- (b) Explain the operation of Thyristor Controlled Series Capacitor with the help of Impedance Vs delay angle α Characteristics. **07**
- Q.3** (a) Explain two-machine (two-bus) transmission model of power system with an ideal midpoint Reactive Compensator. Draw necessary circuit and diagram in support. **07**
- (b) Explain Thyristor Controlled Reactor with necessary circuit. In context with the same also draw (i) firing angle delay control and (ii) operating waveforms. **07**
- OR**
- Q.3** (a) Describe applications of Flexible AC Transmission System controller in distribution system. Also list and briefly describe the Power Quality problems related to same. **07**
- (b) Explain Thyristor Switched Capacitor and condition for Transient Free Operation with necessary circuit and all associated waveforms. **07**
- Q.4** (a) State importance of a Static Var Compensator configuration. Explain the same with necessary circuit and waveforms. **07**
- (b) Draw a basic block diagram for Static Var Compensator controller incorporating voltage regulator. Also explain function/ working of each block. **07**
- OR**
- Q.4** (a) Explain Fixed Capacitor-Thyristor Controlled reactor type Var Generator. Draw only neat and labeled functional control scheme for the same. **07**

- (b) List and discuss issues related to Voltage Regulator Design with respect to Static Var Compensator. **07**
- Q.5** (a) List and justify advantages of Static Synchronous Compensator over Static Var Compensator and Synchronous Condenser. Draw necessary diagram in support. **07**
- (b) Draw a neat and labeled circuit for Gate Turn Off Thyristor based three phase Six Pulse Static Synchronous Compensator. Write mathematical expression in support. **07**
- OR**
- Q.5** (a) Draw (i) ideal V-I Characteristics and (ii) function block diagram related to dynamic behavior of the Static Compensator. List important outcome from the same. **07**
- (b) Explain significance of a Twelve Pulse Static Synchronous Compensator. Draw necessary relevant circuit and waveforms in support. **07**
