Enrolment No.____

GUJARAT TECHNOLOGICAL UNIVERSITY

| M.E. SEMESTER III–EXAMINATION (Remedial)– WINTER 2015 | | | | |
|---|-------------|--|----------|--|
| Subject code: 734502Date: 07/12Subject Name: EMC in Power ElectronicsTotal MarksTime: 2:30 PM to 5:00 PMTotal Marks | | | | |
| | | | | |
| | | Make suitable assumptions wherever necessary. | | |
| | | Figures to the right indicate full marks. | | |
| | | | | |
| Q.1 | (a) (b) | Explain spectrum analyzers in detail. Discuss the sources of EMI generation in detail. | 07 07 | |
| Q.2 | (a) | Explain basic terms and conducted EMI references with reference to EMI measurement. | 07 | |
| | (b) | Explain Laplace transform root calculation method. OR | 07 | |
| | (b) | Derive the equations of insertion loss of two port network in terms of Z parameters and ABCD parameters. | 07 | |
| Q.3 | (a) (b) | Describe shielded transformers with necessary equivalent circuit. Draw equivalent circuit for determining the capacitive current of noise suppression and explain it with necessary equation. OR | 07 07 | |
| Q.3 | (a) (b) | Describe series injection method of worst-case insertion loss test method. Explain the application of RC- Snubber to power semiconductors. | 07 07 | |
| Q.4 | (a) (b) | Explain the method for measuring interference current. Write a short note on damped EMI filter for low current ratings. OR | 07 07 | |
| Q.4 | (a) (b) | Describe impulse voltage withstand test with necessary diagram. Explain feed through capacitor and feed through filter. | 07 07 | |
| Q.5 | (a) (b) | Explain the method for calculating energy content of transient disturbances. Briefly explain the surge protection devices. OR | 07 07 | |
| Q.5 | (a) | Explain circuit balancing method of reduction of electromagnetic coupling reduction. | 07 | |
| | (b) | Explain wiring layout method to reduce EMI coupling. | 07 | |