Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

PDDC - SEMESTER-II EXAMINATION - SUMMER 2016

Subject Code: X20902 Date: 02/06/2016

Subject Name: ELECTRICAL MEASUREMENT I & II

Time:10:30 AM to 01:00 PM Total Marks: 70

Instructions:

- 1. Attempt any five questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a)	Describe the working of Hay's bridge for measurement of Inductance. Derive equation for balance and draw the phasor diagram of bridge under balance conditions.	07
	(b)	Define following terms (i) Sensitivity (ii) Precision(iii) Hysteresis (iv) Drift	07
Q.2	(a) (b)	Explain various effects with which deflecting torque is produced? Derive the dimensions of the following quantities in L,M,T,I units: 1. Potential Gradient 2. Capacitance 3. Magnetic Flux Density	07 07
Q.3	(a)	Explain how the current range of a PMMC instrument can be extended? Also derive equation for shunt.	07
	(b)	Which are the different methods of power measurement in 1-ph and 3-ph systems.	07
Q.4	(a)	Draw the circuit diagram of Schering bridge and derive expression for C and tanδ at balance for dielectric under test.	07
	(b)	Construction and working of D'Arsonval galvanometer.	07
Q.5	(a) (b)	Explain construction and working of Anderson bridge. Explain working of digital LCR meter.	07 07
	(6)	Explain working of digital DelCineter.	U7
Q.6	(a)	Explain Gall Tinsley type A.C. Potentiometer	07
	(b)	Describe different methods of damping with measuring instruments	07
Q .7	(a)	Explain Tri vector meter with a neat diagram.	07
	(b)	With neat sketch explain the two-wattmeter method of power measurement	07
