

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-III EXAMINATION – SUMMER 2016

Subject Code: X30901**Date: 26/05/2016****Subject Name: Basic Electronics****Time: 02:30 PM to 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain V-I characteristics of P-N junction diode. 7
(b) Define the following terms: (i) Potential (ii) ev unit of energy (iii) Volt-equivalent temperature (iv) Thermal resistance (v) Intermodulation distortion (vi) Mean life time of a carrier (vii) Peak Inverse Voltage. 7
- OR**
- Q.2** (a) Define the rectification and describe the full wave bridge rectifier with the help of neat circuit diagram and waveforms. 7
(b) With circuit diagram and characteristics, explain input and output characteristics of transistor in common base mode. 7
- OR**
- (b) Explain how D.C. load line is drawn on input characteristics of CE transistor configuration and state its importance. 7
- Q.3** (a) Define α and β in transistor and relation between α and β . 7
(b) Give a Comparison of CB, CC, CE transistor configuration. 7
- OR**
- Q.3** (a) Explain Voltage divider biasing method for transistor and prove the stability factor $S=1$ for voltage divider biasing method. 7
(b) Explain DC load line and Q-point for any transistor configuration. Also state the necessity of biasing and list biasing methods for transistor. 7
- Q.4** (a) Explain procedure to determine h-parameter h_{fe} , h_{oe} of transistor from static output characteristics. 7
(b) Define stabilization factors: S , S' , and S'' . Derive expressions for S and S' for self-bias transistor circuit. 7
- OR**
- Q.4** (a) Draw a structure of p-channel MOSFET. Explain its working for enhancement type. Also draw and explain drain characteristics and transfer curve for the same device. 7
(b) Define thermal runaway. Derive necessary condition to avoid thermal runaway. 7
- Q.5** (a) Derive an expression for voltage gain (A_V) for CS amplifier with an bypassed source resistance R_S . 7
(b) Determine h-parameters for the two port network. Also draw the hybrid model for CE, CB and CC configurations. 7
- OR**
- Q.5** (a) List the basic configurations of a low frequency FET amplifier. Explain any one of them with the help of neat circuit diagram and small signal equivalent circuit. 7
(b) Draw class B push-pull system and show that the maximum conversion efficiency (η) is 78.5 % for this system. 7
