Seat	No.:	
Scat	110	

Enrolment No.\_\_\_\_\_

## **GUJARAT TECHNOLOGICAL UNIVERSITY** PDDC - SEMESTER-IV EXAMINATION – SUMMER 2016

Subject Code:X41103		ct Code:X41103 Date:01/06/20 ct Name:Integrated Circuits and Applications	Date:01/06/2016	
Ti	•	10:30 AM TO 01:00 PM Total Marks:	70	
	-	<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> <li>Figures to the right indicate full marks.</li> </ol>		
Q.1	(a)	Derive the expression for voltage gain, input resistance, output resistance and bandwidth of Inverting amplifier using non ideal op-amp.	07	
	(b)	Define the following electrical parameters of op-amp: Input offset voltage, Input offset current, Input bias current, CMRR, PSRR, Equivalent input noise voltage and current, Slew rate.	07	
Q.2	(a)	What is an instrumentation amplifier? Explain with the help of neat diagram the operation of an instrumentation amplifier employing three basic Op-amps and with provision for variation in the voltage gain.	07	
	<b>(b)</b>	Draw and explain the circuit diagram for $Vo = V1 + V2 - V3 - V4$ by using Op-amp.	07	
		OR		
	(b)	Draw and explain the Schmitt trigger comparator circuit with hysteresis width of 6V by using Op-amp. (+/-Vsat = +/- $12V$ )	07	
Q.3	(a)	Draw and explain the circuit diagram of full wave rectifier by using Op-amp. How is it better in performance compared to full wave rectifier circuit without Op - amp.	07	
	(b)	Design a differentiator to differentiate an input signal that varies in frequency fro 10 Hz to about 1 KHz.	07	
Q.3	(a)	<b>OR</b> Draw and Explain Working Op-amp based log amplifier	07	
Q.5	( <b>b</b> )	<ul><li>(i) What is thermal drift? How does it affect the performance of an Op-amp circuit?</li><li>(ii) What is error voltage? How can it be reduced?</li></ul>	07	
Q.4	(a)	Analyze second order Butterworth High Pass filter. Draw its frequency response	07	
	(b)	and state design procedure. Draw block diagram of the PLL system and explain function of each block. State the applications of PLL.	07	
0.4	(-)	OR	07	
Q.4	(a) (b)	Draw and explain the circuit diagram of all pass filter by using Op-amp. Draw and explain the circuit diagram for voltage to current converter by using Op-amp with floating load as well as grounded load	07 07	
Q.5	<b>(a)</b>	Design an astable multivibrator for an output frequency of 5 KHz and duty	07	
	(b)	cycle 40%. Consider C=0.047 μF. What are the different types of voltage regulators? Discuss LM317 based adjustable voltage regulator. Indicate bypass capacitors to improve transient response and protective diodes in the connection diagram. <b>OR</b>	07	

- **Q.5** (a) Explain working of monostable multivibrator using IC 555 with internal blocks. Mention applications of monostable using 555 timer.
  - (b) Draw and explain the circuit diagram of Op-amp based voltage limiter as well 07 as clipper circuits.

\*\*\*\*\*