GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-V. EXAMINATION – SUMMER 2016 Subject Code:X50903 Date:06/05/2016 Subject Name:Power Electronics-II			
Time:02:30 PM to 05:00 PM Total Mark			70
<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> <li>Figures to the right indicate full marks.</li> </ol>			
Q.1	(a) (b)	Compare voltage source inverters with current source inverters. Discuss selected harmonic elimination PWM technique.	07 07
Q.2	<b>(a)</b>	Discuss three phase bridge inverters with $120^{\circ}$ conduction. Draw waveforms of line voltage and phase voltage.	07
	(b)	Discuss principle of voltage control of three phase inverter. OR	07
	<b>(b</b> )	Explain current source inverter and its applications.	07
Q.3	(a) (b)	Discuss operation of three phase full wave controllers with Y connected load. Discuss basic principle of matrix converter. <b>OR</b>	07 07
Q.3	(a) (b)	Explain operation of single phase electronic transformer connection changers. Explain single phase full wave controllers with R-L load.	07 07
Q.4	(a) (b)	Discuss operation of load commutated cyclo converter. Discuss sine PWM technique. For carrier to modulation frequency ratio of 15, draw harmonic spectrum. <b>OR</b>	07 07
Q.4	(a)	Explain working principle of three phase cyclo converter. Mention its	07
	(b)	applications. Explain SVPWM technique. Mention its advantages over other PWM technique.	07
Q.5	(a) (b)	Discuss V/f control of induction motor drive. Explain use of AC converter in static VAR compensator.	07 07
		OR	
Q.5	(a) (b)	Explain AC motor operation with non sinusoidal supply waveform. Explain synchronous motor drive with load commutated thyristor inverter.	07 07

\*\*\*\*\*