

GUJARAT TECHNOLOGICAL UNIVERSITY
PDDC - SEMESTER-III EXAMINATION – WINTER 2015

Subject Code: X30901**Date: 18/12/2015****Subject Name: Basic Electronics****Time: 10:30pm to 01:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1(a)** Explain the comparison between half wave rectifier, full wave rectifier with centre tap and full wave bridge rectifier. 7
- (b) State and explain electrical properties of Ge(Germanium) and Si(Silicon). 7
- Q.2(a)** Explain the forward and reverse bias characteristics of P-N junction diode. Also explain its current components during forward and reverse bias. 7
- (b) Explain 'Zener diode' as a voltage regulator. 7
- OR
- (b) Explain Class A and Class b transistor amplifier. 7
- Q.3(a)** Explain full wave rectifier circuit with centre tap and derive its output equation. 7
- (b) Explain h-parameters for CE configuration. 7
- OR
- Q.3(a)** Explain the energy band theory of crystals, insulators, semiconductors and metals with necessary diagrams. 7
- (b) Explain, what is pinch off voltage? Discuss V-I characteristics of FET. 7
- Q.4(a)** Discuss comparison of CB, CE and CC configuration of transistor amplifiers. 7
- (b) Explain transformer coupled audio power amplifier in detail. 7
- ORs
- Q.4(a)** Explain tunnel diode with its characteristics in detail. 7
- (b) Write a short note on Hall effect. 7
- Q.5(a)** Explain working and construction of MOSFET. 7
- (b) Write a short note on clipping circuit with necessary waveform. 7
- OR
- Q.5(a)** Explain 'Drift Current' and 'Diffusion Current'. 7
- (b) Explain the formation of n-type and p-type semiconductors. 7
