Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

PDDC - SEMESTER-III EXAMINATION - WINTER 2015

Subject Code:X30902		Code:X30902 Date:21/12/201	Date:21/12/2015	
Ti	_	Name:Analog & Digital Electronics 0:30pm to 01:00pm Total Marks:	70	
IIIS	1. 2.	Attempt all questions.		
Q.1	(a)	Write down about any seven characteristics of an ideal & a practical Op Amp.	07	
	(b)	Draw the block diagram representation of a typical operational amplifier and justify the significance of each block. Also plot the transfer characteristics of an Op Amp.	07	
Q.2	(a) (b)	Design an Op Amp circuit for obtaining $V_0=V_1-2V_2$. Derive the equation of time period for IC 555 in astable mode of operation. OR	07 07	
	(b)	Derive the equation of time period for IC 555 in monostable mode of operation.	07	
Q.3	(a)	Define minterms, maxterms, Product of Sums and Sum of Products. Simplify (B + BC).(B + B'C).	07	
	(b)	What are binary numbers? How are they different from BCD numbers? List all 4 digit binary and BCD numbers. OR	07	
Q.3	(a)	(1) A (B + C) =	07	
	(b)	(7) 1.1 = Draw the equivalent circuit of an AND gate using NOR gate & an OR gate using NAND gates only.	07	
Q.4	(a)	Do as directed: (1) Convert $4B00_{16}=()_8=()_4=()_2=()_{10}$ (2) Given $(16)_{10}=(10000)_b$, find the value of b.	07	
	(b)	(1) A+BC =	07	
Q.4	(a)	Using K map technique, minimize	07	
		(1) $G(A,B,C) = \sum m(0,1,2) + d(3,5)$ (2) $G(A,B,C) = \sum m(4) + d(6,7)$		
	(b)	Implement a half Adder/ half Subtractor circuit with its truth table and circuit.	07	

Q.5	(a)	Define Flip flop. Classify Flip flop circuits. Explain in details about any one of	07
	(b)	them. Define Counter Classify Counters Explain any one of them in details	07
	(D)	Define Counter. Classify Counters. Explain any one of them in details. OR	U/
Q.5	(a)	Draw the block diagrams of encoders, decoders, multiplexers and de multiplexers with their truth tables.	07
	(b)	Define Shift Registers. Classify all the types of shift registers. Explain any one of them.	07
