Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

## PDDC - SEMESTER-IV EXAMINATION - WINTER 2015

Subject Code:X41103 Subject Name: Integrated Circuits and Applications Time: 02:30pm to 05:00pm Instructions:  1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.			
Q.2	(a)	Design amplifier circuit by using Op-amp 741 such that it can amplify output signal which is 10 times than the input signal with same phase. Find out the factor by which amplifier can increase bandwidth than open loop configuration. (Open loop gain $A = 200,000$ and Open loop bandwidth fo = 5 Hz)	07
	<b>(b)</b>	An Op-amp has slew rate of 1 V/ $\mu$ S with gain of 40 dB. If this amplifier has to faithfully amplify sinusoidal signals from zero to 20 KHz without any distortion what must be maximum input signal level.  OR	07
	<b>(b)</b>	Explain triangle wave generator using Op-amp in detail.	07
Q.3	(a)	The Op-amp is used as an inverting amplifier with following specification: $\frac{\Delta Vio}{\Delta T} = 30 \frac{\mu V}{^{\circ}C} \text{ maximum} \qquad \frac{\Delta Iio}{\Delta T} = 300 \frac{pA}{^{\circ}C} \text{ maximum}$ R1 = 1 K $\Omega$ , RF = 100 K $\Omega$ and RL = 10 K $\Omega$ Vs = +/- 15 V. Assume that the amplifier is nulled at 25° C. Calculate the value of error voltage Ev and the output voltage ate 35° C if:  (a) Vin = 1 mV dc (b) Vin = 10 mV dc.	07
	<b>(b)</b>	Draw and explain the positive and negative clipper circuit using Op-amp.	07
Q.3	(a)	OR  Draw and explain the circuit diagram by using Op-amp which can perform the following task: $Vo = 0$ if $Vin > 0$ $Vo = -Vin$ if $Vin < 0$	07
	<b>(b)</b>	Explain Op-amp based inverting comparator circuit with (i) Positive reference voltage (ii) Negative reference voltage. Show the necessary waveform.	07
Q.4	(a)	What is the difference between active and passive filters? Classify filters based on roll off factors, operating range, and frequency response.	07
	<b>(b)</b>	What is the application of sample and hold circuit? Draw and explain the working of sample and hold circuit.  OR	07
		OR .	

Q.4	(a)	Analyze second order Butterworth High Pass filter. Draw its frequency response and state design procedure.	07
	<b>(b)</b>	If $V_1$ and $V_2$ are two input voltages and $V_o$ is the output voltage then design the circuit diagram with the Op-amp that gives the output voltage $V_o = 2V_1 - 2V_2$	07
Q.5	(a)	Explain the adjustable voltage regulator in detail.	07
	<b>(b)</b>	Explain astable multivibrator using 555 timer in detail.	07
		OR	
Q.5	(a)	Explain 555 timer as a monostable multivibrator in detail.	07
	<b>(b)</b>	List the applications of Operational tranconductance amplifier. Explain its application as a current controlled Integrator.	07

\*\*\*\*\*