Seat No.:	Enrolment No.
Jean 110	E moment 10

Subject Code:X50903

GUJARAT TECHNOLOGICAL UNIVERSITY PDDC - SEMESTER-V EXAMINATION – WINTER 2015

Date:05/12/2015

Subject Name: POWER ELECTRONICS-II Time: 10:30pm to 01:00pm **Total Marks: 70 Instructions:** 1. Attempt all questions. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Sketch the circuit diagram of Parallel Inverter. Explain how class-B commutation is 7 0.1 used and sketch necessary waveforms. Discuss the, Working of the circuit and its advantages. Draw and explain the series Inverter circuit employing Class-A type commutation. Draw and discuss the important waveforms. Explain the working of Mac-Murray Bedford inverter circuit with waveforms, Describe 0.2 (a) each interval of operation. **(b)** Differentiate voltage source inverter with current source inverter. 7 Give the comparison between On/Off control and phase control of A.C voltage 7 controller. 0.3 List the commonly used PWM technique for voltage waveform and control of inverter. 7 Explain any one in details. Explain the principle of operation of three phase bridge inverter with 120 ° conduction 7 **(b)** mode with necessary circuit diagram and waveforms. Draw the neat circuit diagram of three phase full wave bidirectional AC Voltage 7 Q.3 controller and explain it's working with waveforms for different firing angles. Name the different methods of speed control of 3-Ø Induction motor. Explain the 7 principle of speed control of it by PWM method **Q.4** Describe using a neat circuit diagram, waveform and operation of PWM inverter and 7 also explain how the output voltage can be controlled in this scheme. Explain the operation of a single phase voltage controller supplying R-L load when the 7 firing angle " α " is (1) less than the load angle Φ (2) equal to load angle Φ (3) greater than load angle Φ . State the various points of comparisons and their choice/criterion for selection between 7 0.4 (a) AC and DC drives. Draw the torque speed characteristics of 3 phase Induction motor and explain the following regions. (1). Plugging (2). Motoring Explain V/f control of induction motor drives? Give its merits and demerits 7 **Q.5** (a) Describe the basic principle of single phase to single phase cycloconverter for both 7 **(b)** Continues and discontinues conduction for bridge type Cycloconverter. OR Q.5 Describe HVDC transmission system with neat schematic diagram. 7 (a) What is cycloconverter? Explain the principle of operation of cycloconverters and 7 **(b)** discuss the effect of source and load inductances on cycloconverter.
